
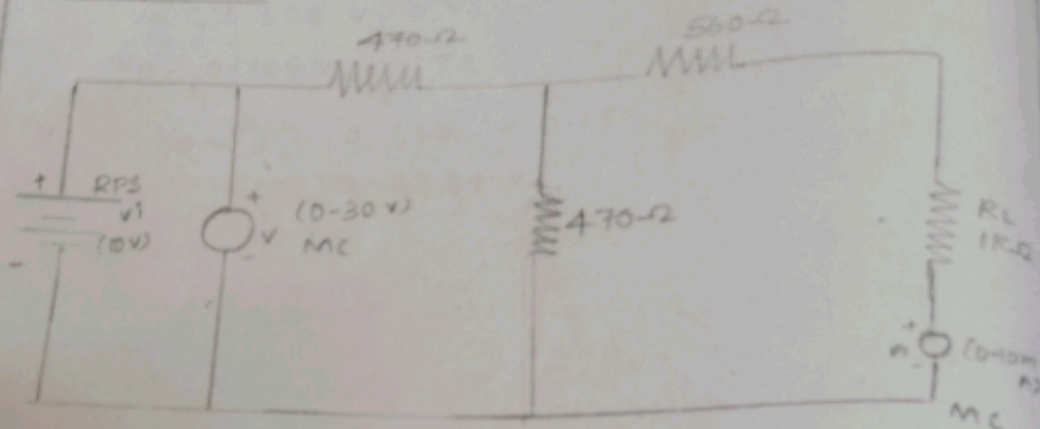


# CIRCUIT DIAGRAM: VERIFICATION OF THEVENIN'S THEOREM


To measure  $I_L$ :

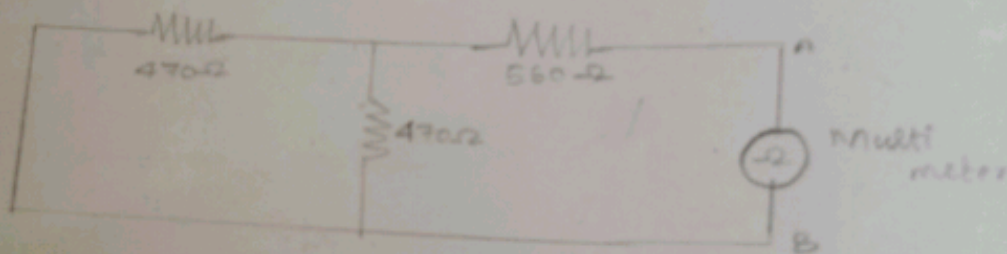


To measure  $R_{Th}$  or  $R_g$



To measure  $V_{Th}$  or  $V_{oc}$

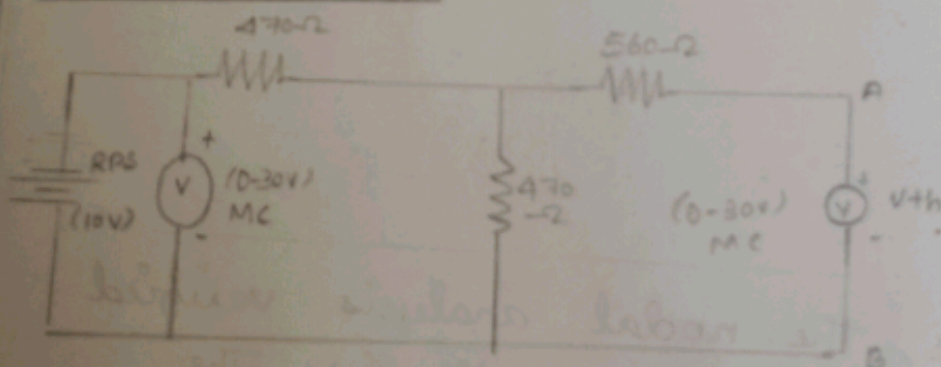

Thevenin's equivalent circuit:

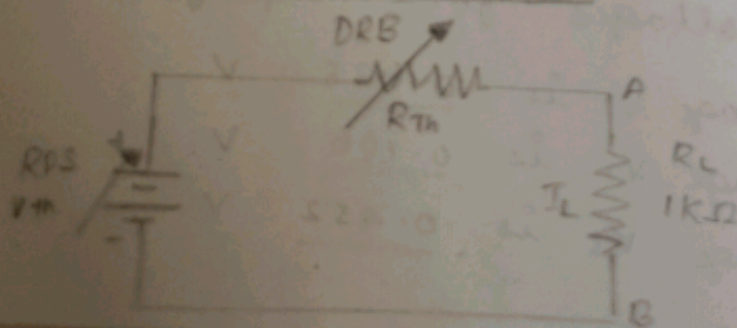

EXP NO: 4

DATE: 19-09-25

AIM:

To

and

APPARATUS:

SL

NO

1.

2.

3.

4.

5.

6.

EXP NO: 4

DATE:  
19.09.25VERIFICATION OF THEVENIN'S  
THEOREMAIM:

To verify Thevenin's theorem practically and theoretically for the given DC circuit.

APPARATUS REQUIRED:

SL. NO	APPARATUS	SPECIFICATION	QUANTITY
1.	Regulated Power Supply (RPS)	(0-30) V	1
2.	Voltmeter	(0-30 V) MC	1
3.	Ammeter	(0-10 mA) MC	1
4.	Resistor	470- $\Omega$ , 560- $\Omega$ 1K- $\Omega$	2, 1, 1
5.	Bread Board	-	1
6.	Multimeter	-	1



TABULAR COLUMN: 1

To measure  $I_L$

$V_i$ (volt)	$I_L$ (amps)
10	286 mA

TABULAR COLUMN: 2

To measure  $R_{th}$  or  $R_N$

From circuit diagram 2,

$$R_{th} = 797 \Omega$$

TABULAR COLUMN: 3

To measure  $V_{th}$  or  $V_{oc}$

$V_i$ (volts)	$V_{th}$ (volts)
10	5V

MODEL CALCULATION:

Practical value of  $I_L$  (from tabulation) = 2.3 mA  
Verification of Thevenin's theorem

$$I_L = V_{th} / (R_{th} + R_L) = 2.22 \text{ mA}$$

Theoretical calculation of  $I_L$ ,  $R_{th}$  ( $R_N$ ) and  $V_{th}$  for the given circuit.



### PROCEDURE:

1. Make the connections as per the circuit diagram : 1
2. Vary the RPS and set an input voltage of 10V.
3. Note down the voltmeter reading ( $V_i$ ) and ammeter reading ( $I_L$ ) in Tabular column 1.
4. Switch off the supply and make connections for Circuit Diagram 2.
5. Measure the Thevenin's resistance  $R_{Th}$  = Norton's resistance  $R_N$ .
6. Switch off the supply and make connection for circuit diagram 3.
7. Set an input voltage of 10V in the RPS and note down the voltmeter readings  $V_i$  and  $V_{Th}(=V_{oc})$  in tabular columns : 3
8. Switch off the supply and make connection for circuit diagram 4.
9. Set an input voltage of 10V in the RPS and note down the voltmeter reading  $V_i$  and ammeter reading  $I_N (=I_{sc})$  in tabular column 4.



### CALCULATION:

By voltage division rule

$$V_{Th} = \frac{V_s \times R_3}{R_1 + R_3} \quad [\text{No current will flow through } R_2 \text{ when } R_2 \text{ is open circuit}]$$

$$V_{Th} = \frac{10V \times 470\Omega}{(470 + 470)\Omega} = 5V$$

$$V_{Th} = 5V$$

$R_{Th}$ :  $R_1$  and  $R_3$  in parallel when voltage source is short circuited.

$$R_{Th} = \frac{470 \times 470}{470 + 470} + 560 = 255 + 560 = 795\Omega$$

$$R_{Th} = 795\Omega$$

Finding  $I_L$ :

$$R_{Th} \text{ in series with } R_L \therefore R_{eq} = R_L + R_{Th} = 1.795K\Omega$$

$$I_L = \frac{V}{R_{eq}} = \frac{5V}{1.795 \times 10^3\Omega} = 2.79mA$$



10. Draw the thevenin's equivalent circuit diagrams and Norton's equivalent circuit as shown in circuit.

11. Calculate the  $I_L$  value using the formula  $I_L = V_{th} / (R_{th} + R_L)$

Norton's theorem

$$I_L = I_N * R_N / (R_N + R_L)$$

12. Theoretically verify the Norton's theorem.

### RESULT:

Thus Thevenin's theorem is verified practically and theoretically.